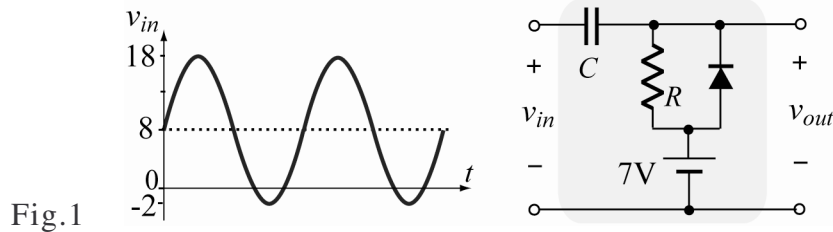


1. (5%) If  $V_{D(ON)}=0.7V$ , draw the output waveform  $v_{out}(t)$



2. (10%) Logic circuits are shown in Fig. 2 and Fig. 3. Write down the Boolean functions of  $Y$  in terms of  $A$  and  $B$ ?

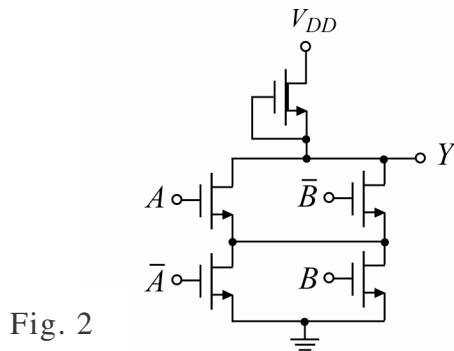


Fig. 2

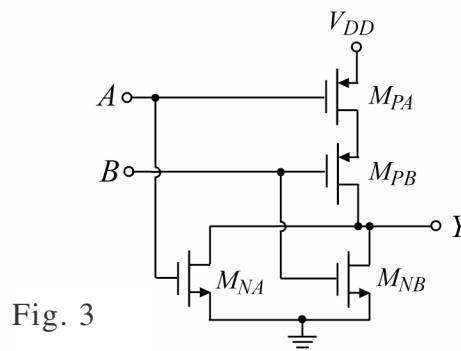


Fig. 3

3. (1) Draw the OP-Amp Wien bridge oscillator circuits with the components  $R_1, R_2, R_3, R_4, C_1$  and  $C_2$ . (5%)

- (2) Determine the resistances ratio of the OP-Amp required (3%), and the oscillation frequency. (2%)

4. Fig. 4 shows a common-emitter circuit. The circuit parameters are :  $\beta=100, R_C=6k\Omega, R_B=50k\Omega, V_{CC}=12V, V_{BB}=1.5V, V_{BE}=0.7V, V_T=26mV, V_A=\infty$  and  $v_i(t)=0.5\sin\omega t(V)$ . Calculate the maximum and minimum values of  $i_C(t)$  and  $v_O(t)$ . (10%) Draw one cycle of the waveforms  $i_C(t)$  and  $v_O(t)$  (5%) .

5. Fig. 5 shows an NMOS IC amplifier with enhancement load. The parameters are :  $V_{T1}=1V, V_{T2}=2V, W_1=45\mu m, W_2=24\mu m, L_1=5\mu m, L_2=6\mu m$ , and  $\mu_n C_{ox}=100\mu A/V^2$ , where  $V_T, W, L, \mu_n$ , and  $C_{ox}$  are the threshold voltage, the channel width, the channel length, the mobility of the electrons in the inversion layer, and the oxide capacitance per unit area, respectively.

- (1) Calculate the dc bias point ( $V_O$  and  $I_D$ ) with  $V_{DD}=10V, V_{GS}=3V$ . (8%)

- (2) Calculate the small signal voltage gain  $A_v=v_o/v_i$ . (2%)

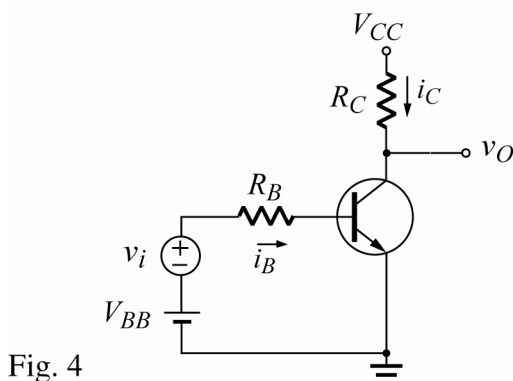


Fig. 4

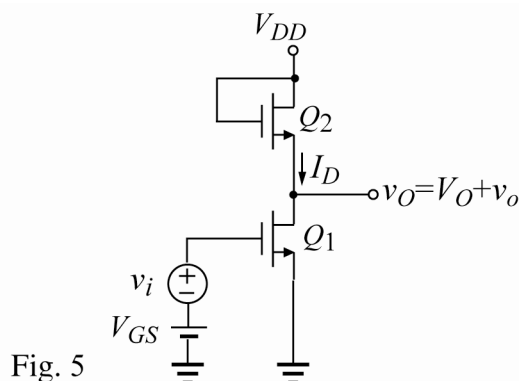


Fig. 5

6.

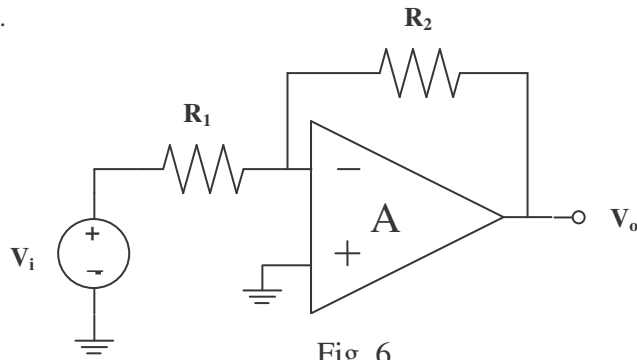


Fig. 6

The circuit shown in Fig. 6 is an inverting amplifier. The resistance of  $R_1$ ,  $R_2$  are  $1\text{k}\Omega$ ,  $10\text{k}\Omega$  respectively. Find the voltage gain  $V_o/V_i$  of this amplifier in each of the following cases.

- (a) OPA gain  $A = \infty$  (3%)
- (b)  $A = 10^5$  (4%)

(c)  $A = A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}} = \frac{10^5}{1 + \frac{s}{2\pi \times 10}}$ , what is the cutoff frequency of this inverting amplifier?

(8%)

7.

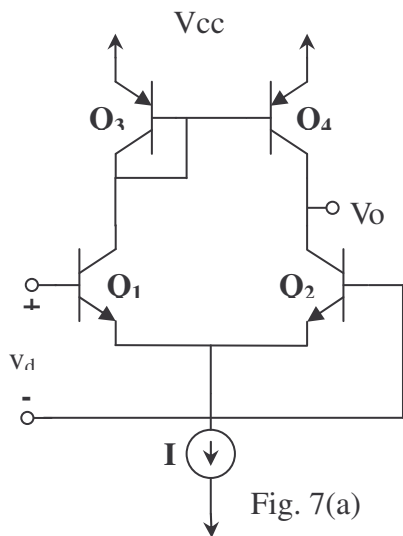


Fig. 7(a)

For the active-loaded differential amplifier of Fig. 7(a) when biased with a current  $I = 0.5\text{ mA}$ , if the transistors has current gain  $\beta = 200$ , Early voltage  $V_A = 100\text{V}$ , suppose the small-signal operation of the amplifier can be modeled by the models shown in Fig. 7(b), find the value of the differential input resistance  $R_i$ , transconductance  $G_m$  and output resistance  $R_o$ . (10%)

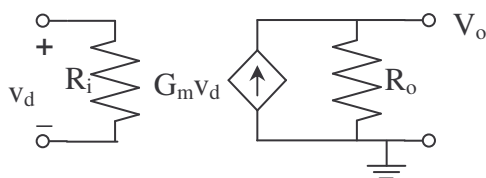


Fig. 7(b)

8.

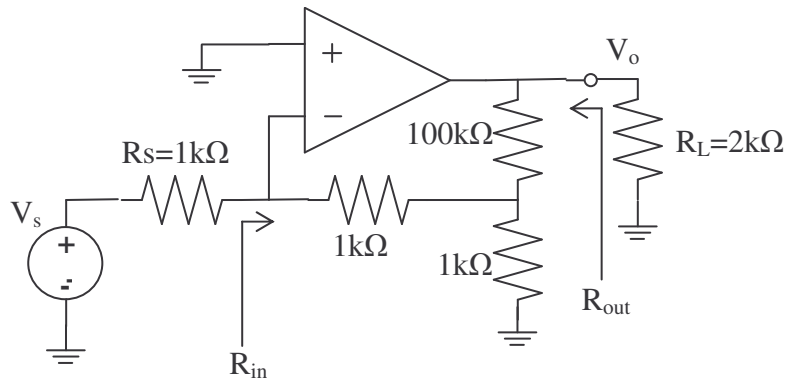


Fig.8

There are four basic feedback topologies of a feedback amplifier. Determine the feedback topology of the circuit displayed in Fig. 8 and find the voltage gain  $V_o/V_s$ , input resistance  $R_{in}$  and output resistance  $R_{out}$  by using the feedback method. The values of the related parameters of the OPA are specified as follows, the

open loop gain  $\mu = 10^4$  V/V,  
differential input resistance  $R_{id} = 100k\Omega$  and output resistance  $r_o = 1k\Omega$ .(15%)

9.

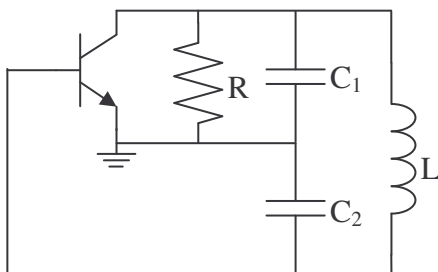


Fig. 9

The circuit in Fig. 9 is a Colpitts oscillator, show that the resonance frequency  $\omega_0$  is

$$\omega_0 = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

(10%)