
 


1. For the circuit in Fig. 1, the NMOS and PMOS transistors are matched with $k'_n(W_n/L_n) = k'_p(W_p/L_p) = 1 \text{ mA/V}^2$ and $V_{tn} = -V_{tp} = 1\text{V}$. Assume $\lambda = 0$ for both devices, find the drain current i_{dn} and the voltage v_o for

 
- (a) $v_i = 0 \text{ V}$. (10%)
 (b) $v_i = 2.5 \text{ V}$. (10%)



2. To design a difference amplifier shown in Fig. 2, we will need to select the resistors properly.
- (a) Find the value of R_4 such that the common-mode gain is 0. (10%)
 (b) Use the same R_4 from (a) and find the differential gain. (5%)



 3. Find the voltage gain (v_o/v_i) of the transistor amplifier shown in Fig. 3 for the small-signal operation. Assume $\beta = 100$. Hint: use the hybrid- π model to represent the BJT as a voltage-controlled current source. (15%)



4. Assume that for the basic CMOS inverter $(W/L)_n = n = 2$, $(W/L)_p = p = 5$ and that channel length is $0.25\mu\text{m}$. For the circuit shown in Fig. 4, find (a) the relation between the output Y and the input signal A, B, C, D (b) (W/L) ratio for each transistor.
 (20%)

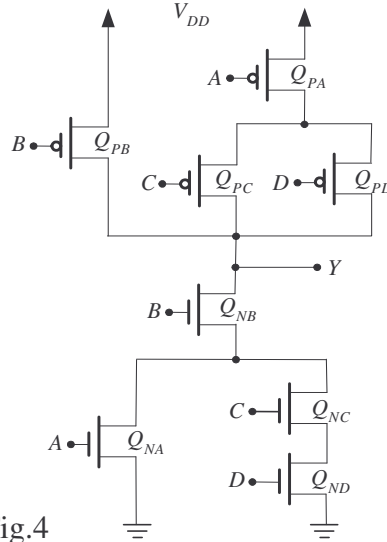


Fig.4

5. For the ideal op amp circuit in Fig.5, (a) what is the circuit? (b) please derive the relation between the v_I and v_O (c) plot the voltage transfer characteristic of the circuit (d) Assume that the op amp has $\pm 12\text{V}$ output saturation levels, $R_1 = 10\text{ K}\Omega$, $R_2 = 40\text{ K}\Omega$ and $v_I = -5\text{V}$, then the voltage of $v_O = ?$
 (20%)

 


Fig.5

6. A multi-pole amplifier has a first pole at 1MHz , second pole at 10MHz and an open-loop gain of 100dB . This amplifier is to be compensated for closed-loop gain as low as 20dB . If the compensation is obtained by moving the first pole, at what frequency must the first new pole be placed?
 (10%)