

1. Consider the parallel-based clipper circuit of Fig. 1 for $R_1=20\text{k}\Omega$, $R_2=10\text{k}\Omega$, $V_1=1.8\text{V}$, $V_2=4.3\text{V}$. Assume diode cut-in voltages of $V_f=0.7\text{V}$. Draw the voltage transfer characteristics curve. (10%)

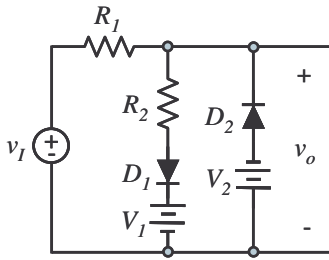


Fig. 1

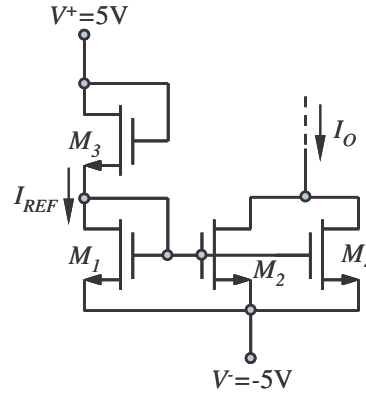


Fig. 2

2. Consider the circuit shown in Fig. 2. The transistor parameters are: the threshold voltage $V_{TN}=2\text{V}$, the conduction parameters $K_{n1}=K_{n2}=K_{n4}=0.25\text{mA/V}^2$, $K_{n3}=0.1\text{mA/V}^2$, and the channel-length parameter $\lambda=0$. Determine I_{REF} and I_O . (10%)
3. For a bipolar transistor, the unity-gain bandwidth is $f_T=2\text{GHz}$ and the low-frequency current gain is $\beta_o=150$. (a) Determine the beta cutoff frequency f_β . (5%) (b) Find the frequency at which the magnitude of the small-signal current gain h_{fe} is 10. (5%)
4. Consider the difference-amplifier circuit of Fig. 3 for the case $R_1=R_3=2\text{k}\Omega$ and $R_2=R_4=200\text{k}\Omega$. (a) Find the value of the differential gain A_d . (5%) (b) Find the value of the differential input resistance R_{id} and the output resistance R_O . (5%) (c) If the resistors have 1% tolerance (i.e. each can be within $\pm 1\%$ of its nominal value), find the worst-case common-mode gain A_{cm} and the corresponding value of CMRR. (5%) (Note: The op amp is ideal.)

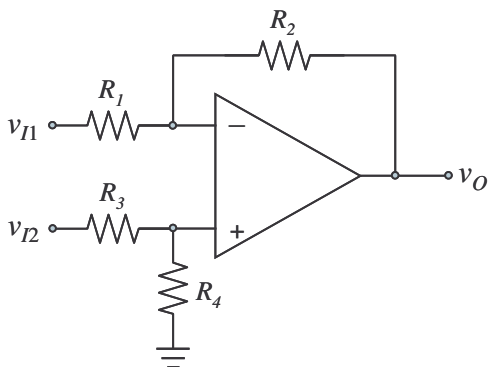


Fig. 3

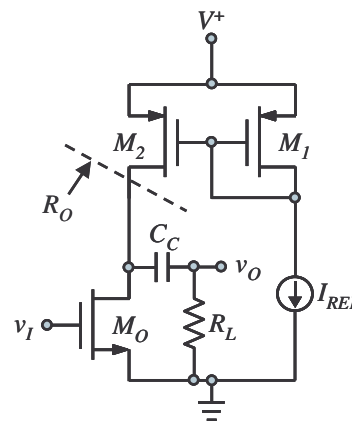


Fig. 4

5. The MOSFET amplifier with active load is shown in Fig. 4. The transistor parameters are: the channel-length parameters $\lambda_n = \lambda_p = 0.01\text{V}^{-1}$, the threshold voltage of n-channel MOSFET $V_{TN} = 1\text{V}$, the threshold voltage of p-channel MOSFET $V_{TP} = -0.5\text{V}$, the conduction parameter of n-channel MOSFET $K_n = 1\text{mA/V}^2$, the conduction parameter of p-channel MOSFET $K_p = 2\text{mA/V}^2$, $R_L = 100\text{k}\Omega$. Assuming M_1 and M_2 are matched and $I_{REF} = 0.5\text{mA}$. (a) Calculate the small-signal equivalent output resistance R_O of active load. (5%) (b) Calculate the small-signal voltage gain. (5%)
6. Consider the cascade circuit in Fig. 5. Let the low-frequency current gain $\beta = 100$, $V_{BE(on)} = 0.7\text{V}$, and Early voltage $V_A = \infty$ for each transistor. Assume $V_{CC} = 12\text{V}$, $R_L = 2\text{k}\Omega$, and $R_E = 0.5\text{k}\Omega$. (a) Find R_C , R_1 , R_2 , and R_3 such that $I_{CQ2} = 0.5\text{mA}$ and $V_{CE1} = V_{CE2} = 4\text{V}$. Let $R_1 + R_2 + R_3 = 100\text{k}\Omega$. (8%) (Hint: Neglect the dc base currents and assume $I_C = I_E$ in both Q_1 and Q_2 .) (b) Determine the small-signal voltage gain $A_v = v_o/v_s$. (7%)

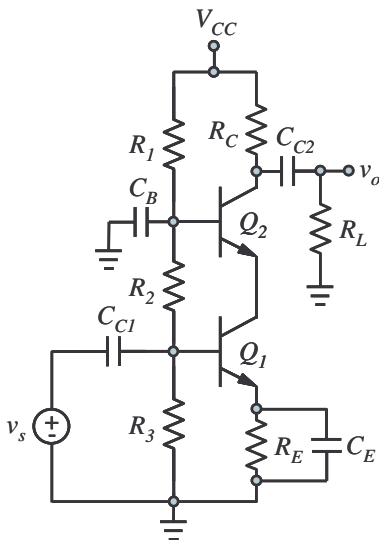


Fig. 5

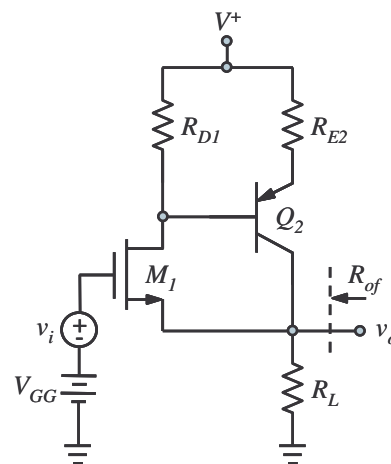


Fig. 6

7. Consider the BiCMOS circuit in Fig. 6. The transistor parameters are: the conduction parameter of n-channel MOSFET $K_n = 0.2\text{mA/V}^2$, the threshold voltage of n-channel MOSFET $V_{TN} = 1\text{V}$, the channel-length parameter $\lambda = 0$ for M_1 ; and the low-frequency current gain $h_{FE} = 100$, the transistor cut-in voltage $V_{EB(on)} = 0.7\text{V}$, the Early voltage $V_A = \infty$ for Q_2 . (a) Find the small-signal voltage gain $A_{vf} = v_o/v_i$. (8%) (b) Determine the output resistance R_{of} . (7%)
8. Consider the astable multivibrator circuit in Fig. 7. Let the op-amp saturation positive and negative saturation voltages are L_+ and L_- , respectively. (a) Draw the waveforms v_o , v_+ , and v_- .

(8%) (b) Find the frequency of oscillation. (7%)

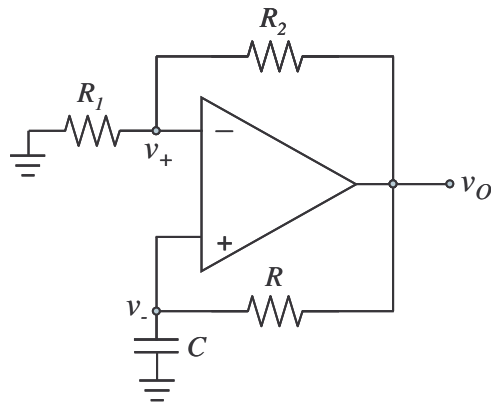


Fig. 7