

1. The input, and output of the network are shown in Fig. 1. Obtain the unknown element values. (20 %)

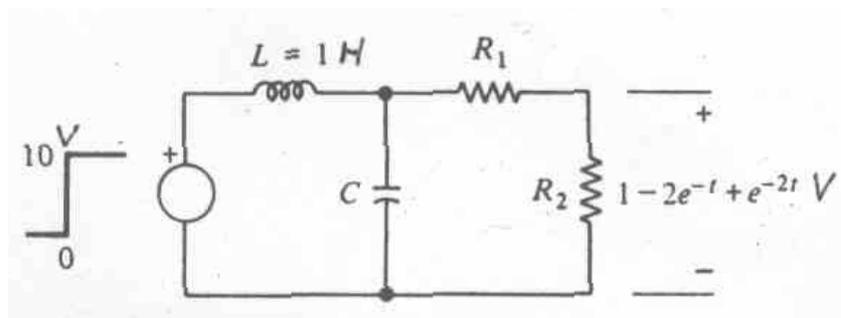


Fig. 1

2. A linearly rising voltage is applied to the RLC network shown in Fig. 2. How much energy is supplied by the source in one second? (20 %)

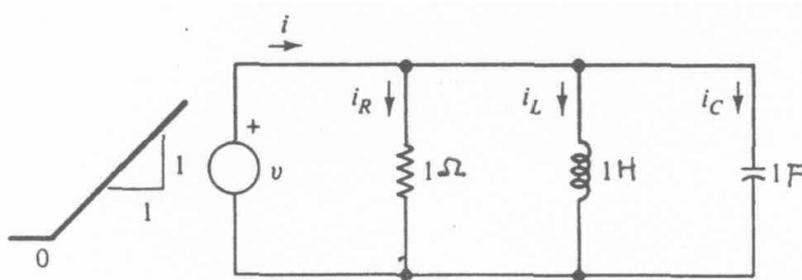


Fig. 2

3. For the circuit in Fig. 3,
- Find the Thevenin equivalent circuit with respect to the terminals a, b for the circuit shown in Fig. 3. (10 %)
 - Find the load impedance Z if maximum average power is delivered to Z. (5 %)
 - Find the maximum average power delivered to Z. (5 %)

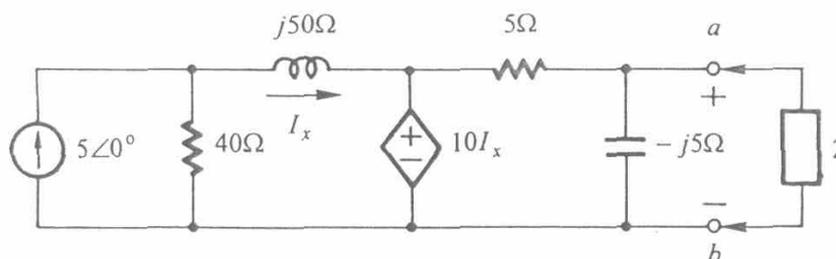


Fig. 3

4. Let $i_s = 5u(-t) - 15u(t)$ in Fig. 4. Find

- (a) $V_R(0^+)$ (5%)
 (b) $\frac{dV_C(0^+)}{dt}$ (5%)
 (c) $\frac{di_L(0^+)}{dt}$ (5%)

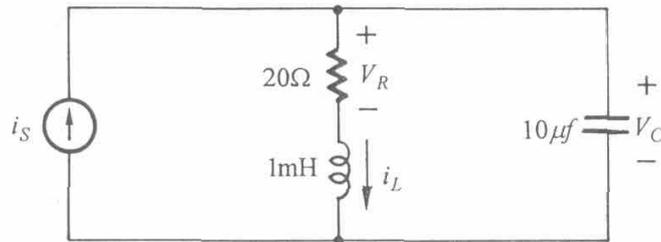


Fig. 4

5. A balanced Y-connected load is supplied by a balanced power system in which $Z = 10 + j10$

Ω , $V_{ab} = 100\sqrt{6} \angle 0^\circ$ Volt, $V_{bc} = 100\sqrt{6} \angle -120^\circ$ and $V_{ca} = 100\sqrt{6} \angle +120^\circ$ Volt. Two wattmeters are arranged to measure the total power received by the load and the circuit is shown in Fig. 5.

- (a) Find the reading value of wattmeter A. (7%)
 (b) Determine the total power absorbed by the load. (8%)

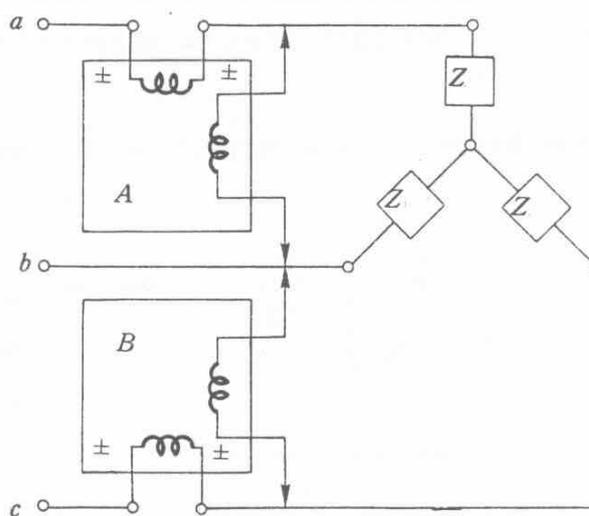


Fig. 5

6. In Fig. 6, R_1 , R_2 , and R_3 are fixed. For what turns ratio is the output voltage maximum?
(10%)

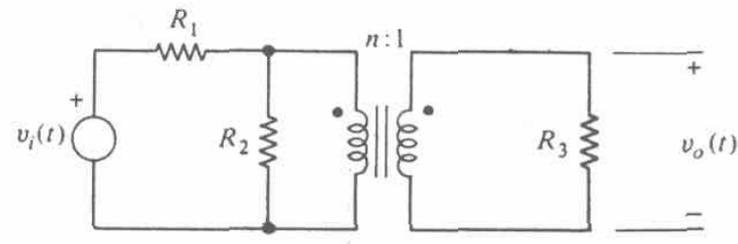


Fig. 6