

1. Choose the correct answer for the following questions. (40%)

- (1) An amplifier has that open voltage gain of +40dB, input resistance of 10KΩ and output resistance of 100Ω, and is used to drive 1 KΩ load. Find the power gain in dB. (A)40 (B)49 (C)80 (D)98 (E)102

- (2) For the ideal opa circuit shown in Fig.1 and $R_1 = 1k\Omega$, $R_2 = 25k\Omega$, $R = 10k\Omega$, find the input resistance R_i in Ω. (A)1k (B)10k (C)25k (D)26k (E)∞

 


Fig.1

- (3) Actually, the tuned amplifier is a (A)High Pass Filter (B)Band Pass Filter (C)Low Pass Filter (D)Notch Filter (E)All Pass Filter.

- (4) For the ideal opa circuit shown in Fig.2 and if the op amp has ±12V output saturation levels, $R_1 = 10k\Omega$, $R_2 = 40k\Omega$. Which is the possible input voltage v_I such that the output voltage will transform from -12V to +12V? (A)-4V (B)-2V (C)0V (D)2V (E)4V

 


Fig.2

- (5) Decide the locations of the zeros from the circuit in Fig.3 and derive that the circuit is a (A)High Pass Filter (B)Band Pass Filter (C) Low Pass Filter (D)Notch Filter (E)All Pass Filter.

 


Fig.3

- (6) A STC network has the following transfer function:

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{100}{s+1}$$

Which statement is correct about this network?

- (A)Corner Frequency: 100 rad/sec
 (B)voltage gain: 100 dB at frequency $\omega = 1$ rad/sec
 (C)dc gain: 40dB
 (D)high frequency gain: 100
 (E)If the frequency is larger than the Corner Frequency, the gain decreases 10dB while the frequency increases 10 times.
- (7) Which amplifier will be on the last stage of multistage amplifier for the consideration of impedance? (A)Common Emitter (B)Common Base (C)Common Collector (D)Common Gate (E)Common Source

- (8) The circuit shown in Fig.4 is a NMOS digital switch under that gate voltage $V_G = V_{DD} = 5V$, the FET with $V_t = 1V$, and the capacitor C is the output load capacitance. The v_I is the input voltage, and v_O is the final output voltage. Which statement in the following is correct? (A)if $v_I = 5V$, then $v_O = 5V$ (B)if $v_I = 5V$, then $v_O = 0V$ (C)if $v_I = 0V$, then $v_O = 0V$ (D)if $v_I = 0V$, then $v_O = 5V$ (E)if $v_I = 2.5V$, then $v_O = 2.5V$
- (9) For the circuit shown in Fig.5, please indicate the resistor that supports the negative feedback for bias. (A) R_1 (B) R_2 (C) R_C (D) R_E (E)both R_1 and R_2
- (10) Which parameters in the following are correct for the normal digital circuits operations?
 (A) $V_{OH} = 3.2V, V_{IH} = 1.8V, V_{OL} = 0.3V, V_{IL} = 0.8V$
 (B) $V_{OH} = 1.8V, V_{IH} = 3.2V, V_{OL} = 0.3V, V_{IL} = 0.8V$
 (C) $V_{OH} = 1.8V, V_{IH} = 3.2V, V_{OL} = 0.8V, V_{IL} = 0.3V$
 (D) $V_{OH} = 3.2V, V_{IH} = 1.8V, V_{OL} = 0.8V, V_{IL} = 0.3V$
 (E) $V_{OH} = 2.8V, V_{IH} = 3.2V, V_{OL} = 0.5V, V_{IL} = 1.0V$

 


Fig.4

 


Fig.5

2. Consider the circuit shown in the Fig.6 with $R = 1K\Omega$. Assume the diode have a $0.7V$ voltage drop at 1 mA current and $n = 2$. The power supply voltage V^+ has a dc value of $12V$ on which is superimposed a $60Hz$ sinusoid of $1V$ peak amplitude. Calculate
 (a)the dc voltage drop of the diode V_D by the iteration (three significant figures), and
 (b)the amplitude of the sine-wave signal \hat{v}_d appearing across the diode.
 (10%)

 


Fig.6

3. The circuit as Fig.7 shows and the transistor has $V_t = 1V$, $k_n'(W/L) = 0.25\text{mA/V}^2$, $V_A = 50V$. If $V_{DD} = 12V$, $R_D = 10K\Omega$, $R_G = 10M\Omega$, $R_L = 10K\Omega$, find
 (a)DC drain current I_D (5%)
 (b)voltage gain. (5%)
 (c)input resistance R_{in} . (5%)
 (d)the largest allowable input signal. (5%)

 


Fig. 7

4. For the circuit shown in Fig.8 under that $V_{CC} = +12V$, $R_C = 6K\Omega$, $R_E = 3K\Omega$, find the highest voltage to which the base can be raised while the transistor remains in the active mode. Assume $\alpha \approx 1$. (10%)

 


Fig.8

5. An active-loaded MOS differential amplifier as shown in Fig.9 is specified as follows: $(W/L)_n = 100$, $(W/L)_p = 60$, $\mu_n C_{ox} = 2\mu_p C_{ox} = 0.2 \text{ mA/V}^2$, $I = 20\mu\text{A}$, $|V_{An}| = |V_{Ap}| = 10V$. If the differential input voltage $v_{id} = v_{G1} - v_{G2}$, calculate differential voltage gain $A_d = v_o/v_{id}$. (10%)

 


Fig.9

6. For the oscillator shown in Fig.10, please use the oscillation principle to derive
 (a) the frequency of oscillation (b) R_2/R_1 for oscillation. (10%)

 


Fig. 10